
 


 Exercise 9 (Synchronizing a PB reset):

- On the FPGA board we have a couple of push button switches. We will use one as the source for our asynchronous reset.
- It is simply a momentary push button switch to ground with a pull-up resistor.

Imagine what a disaster this implementation of a global reset would be!!




Button pushed
(has bounce)

Button released
(RC approach)

When does reset
deassert relative to
clock?

Remember...you want your reset deasserted on the opposite edge of clock that your other flops are active on. This means we want our reset to deassert on the negative edge of clock.

Exercise 9 (Synchronizing a PB reset):

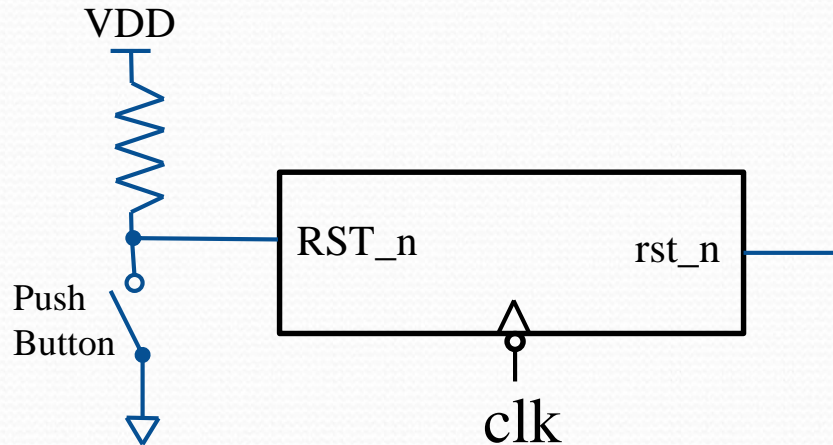


We want to build a reset synchronizer that takes in the raw push button signal and creates a signal that is deasserted at the negative edge of clock.

It will have an interface of:

RST_n = raw input from push button

clk = clock, and we use negative edge

 rst_n = our synchronized output which will form the global reset to the rest of our chip.




Push of the button will asynch reset the two flops. When button is released we have a double flopping (metastability reasons) to produce our global `rst_n`. The flops are negative edge triggered so our global reset will deassert on the opposite edge of all our other flops.

Code this reset synch unit (**rst_synch.v**)

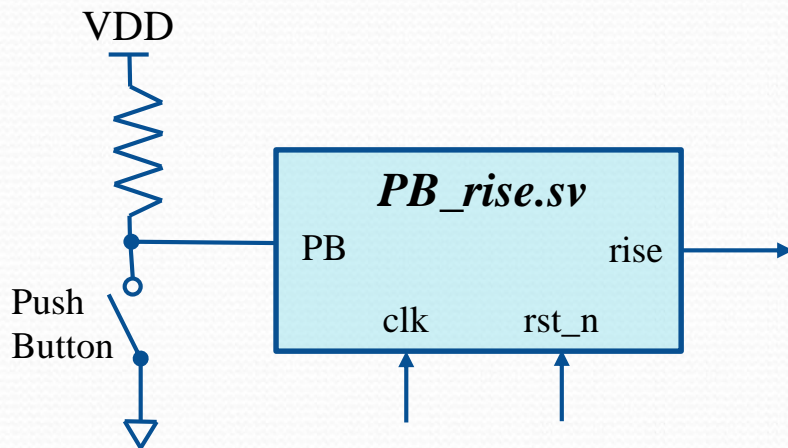Exercise 9 (Synching and Edge Detecting):

- We will also make use of the other push button on the board as a user interface. So we want to make a simple block to synch it (double flop it for meta-stability reasons) and detect a rising edge (release of the button).



Create a block called *PB_rise.sv*.

It should double flop the push button, Then flop it one more time to create a rising edge detector. Outputs a high for 1 clock when a rising edge of PB occurs.

Since the normal state of the PB input is logic 1, should the flops be reset or preset?

Submit: *rst_synch.sv* & *PB_rise.sv* to the dropbox.