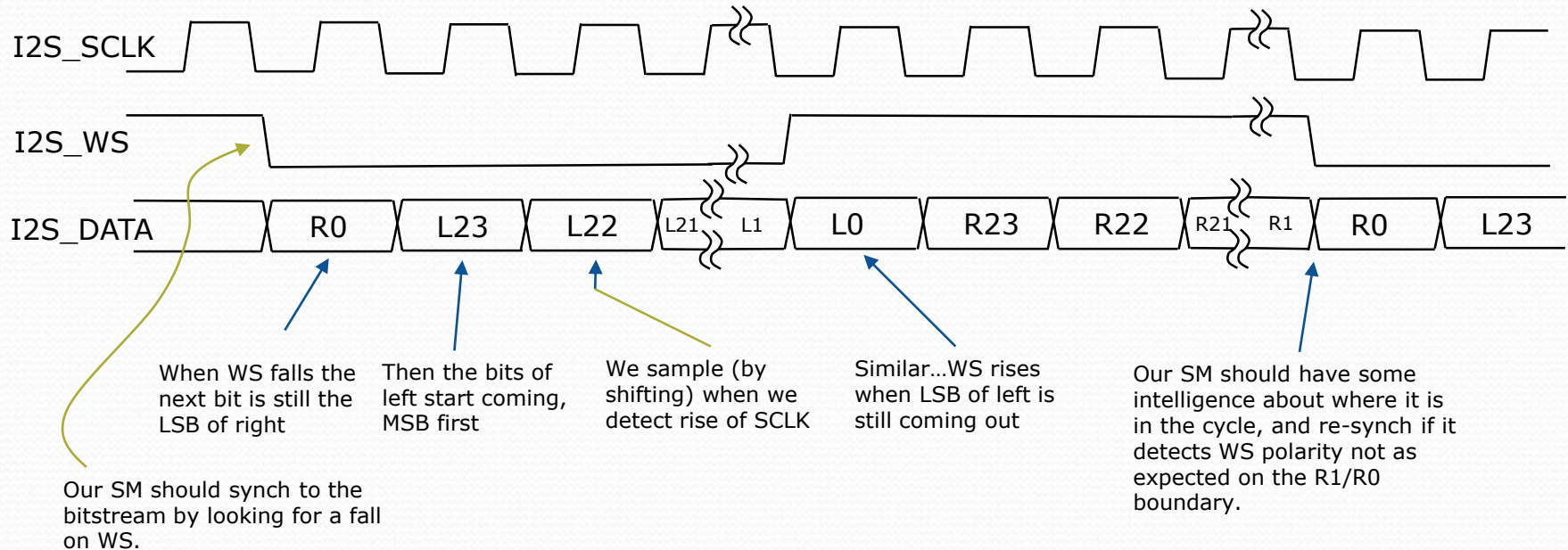




# Exercise 13: I2S\_Slave (HW4 Prob 5).

- I2S is the protocol the RN-52 BT Module will use to output audio. It is quite similar to SPI in many ways, except this time we are the slave and the RN-52 is the master.



- The protocol is 24-bit left/right audio data at 44.1kHz...**SCLK** freq is:  $24 \times 2 \times 44.1k = 2.11\text{MHz}$
- The **WS** line is generally low during left data, and high during right...except it leads by 1 bit.
- We would sample the data by shifting our shift register(s) when we detect **SCLK** rise.
- We initially synched to the stream by looking for the fall of **WS** then ignoring the next **SCLK** rise, and then start shifting in left data on **SCLK** rise.
- When we know we are at **R1** we should check that **WS** is still high. When we know we are at **R0** we should check that **SCLK** is low. If this is not true we should re-synch. Otherwise we would go right back to sampling left data after **R0**.
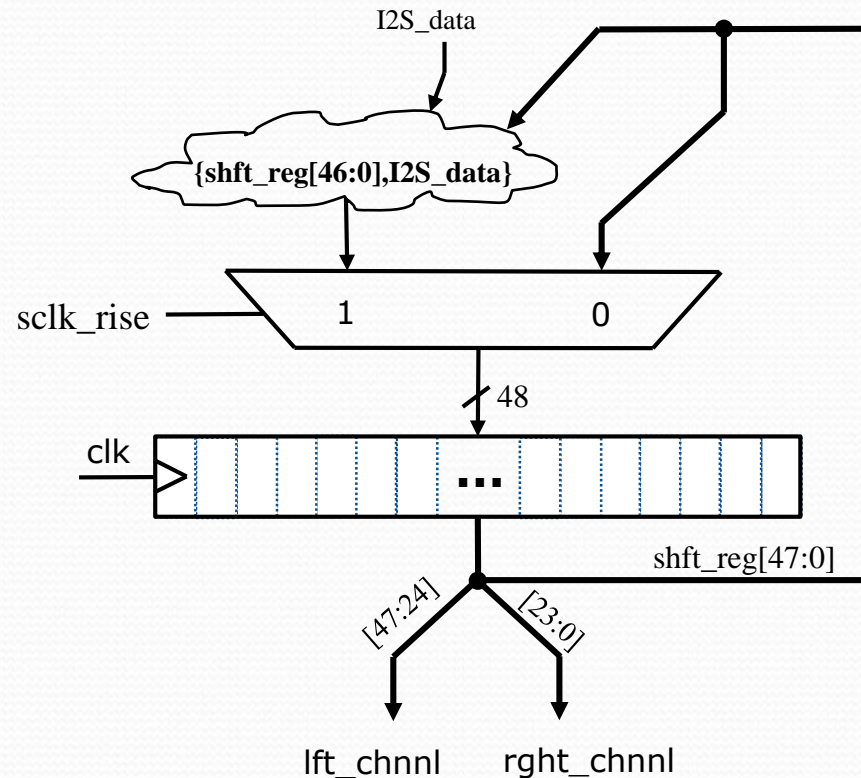 
# Exercise 13: Possible Architecture of I2S Slave



Also need a SM to control it, and assert when the data `{lft_chnnl,rght_chnnl}` is **vld**. **vld** can be a single system clock cycle wide. **lft\_chnnl** and **rght\_chnnl** will get buffered (captured) in registers) elsewhere.




## Exercise 13: I2S\_Slave (HW4 Prob 5).

- Implement a module called **I2S\_Slave.sv** with the following interface:

Signal:	Dir:	Description:
clk,rst_n	In	You know what these are
I2S_sclk	In	This is the SCLK signal of the I2S master. You should shift your shift register when you detect a rising edge on this signal.
I2S_ws	In	Word Select signal from I2S master. Leads bitstream by one bit. Low means left, high means right data
I2S_data	In	Serial data from I2S master. Should be sampled (shifted) into the LSB of a 48-bit shift register
lft_chnnl[23:0]	Out	Parallel 24-bit representation of left audio channel data
rght_chnnl[23:0]	Out	Parallel 24-bit representation of right audio channel data
vld	Out	Only has to be valid for 1 system clock cycle. <b>lft_chnnl</b> and <b>rght_chnnl</b> will be sampled (buffered) in the EQ engine based on this <b>vld</b> signal.
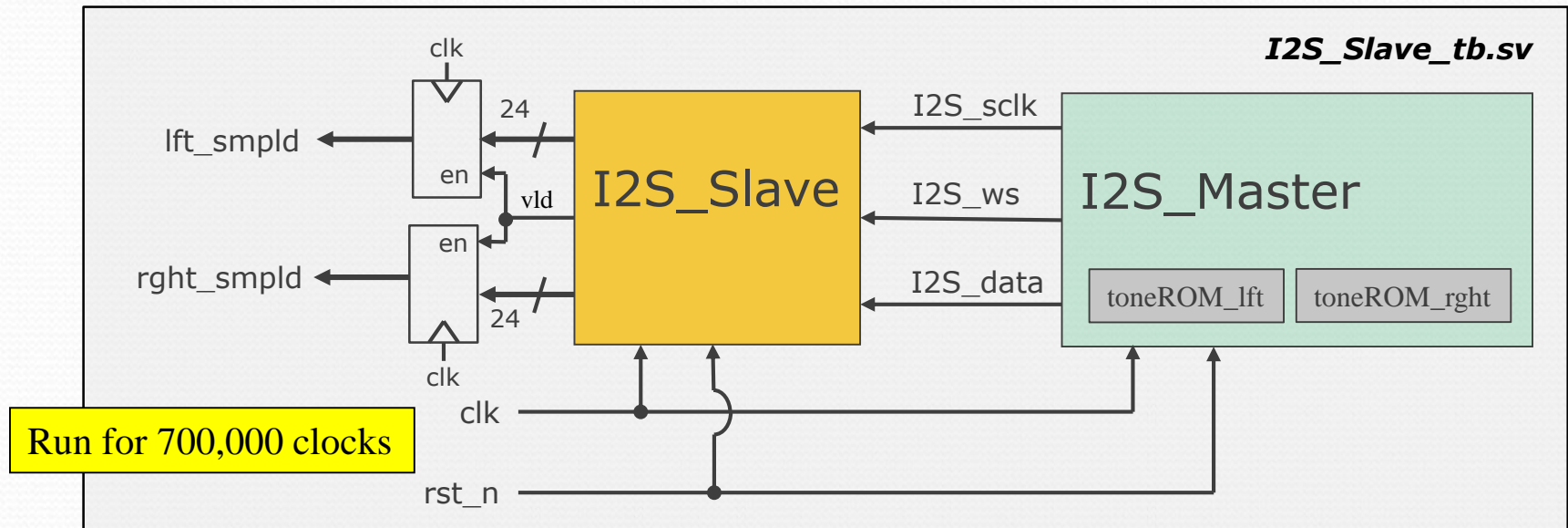
# Exercise 13: Testing I2S\_Slave



- A module called **I2S\_master.sv** is provided on the Canvas page. Use this to help you build a test bench for **I2S\_Slave.sv**



- Build a testbench as you see above. You should have a couple of 24-bit registers sampling the left and right outputs of your slave based on **vld**. One can plot signal in the modelSim viewer as analog. If you have a couple of sinusoids for the smpld values you have it right.
- Turn in: I2S\_Slave.sv, I2S\_Slave\_tb.sv, and a screen shot** showing it worked.


# Exercise 13: Testing I2S\_Slave

## Displaying Signal As Analog

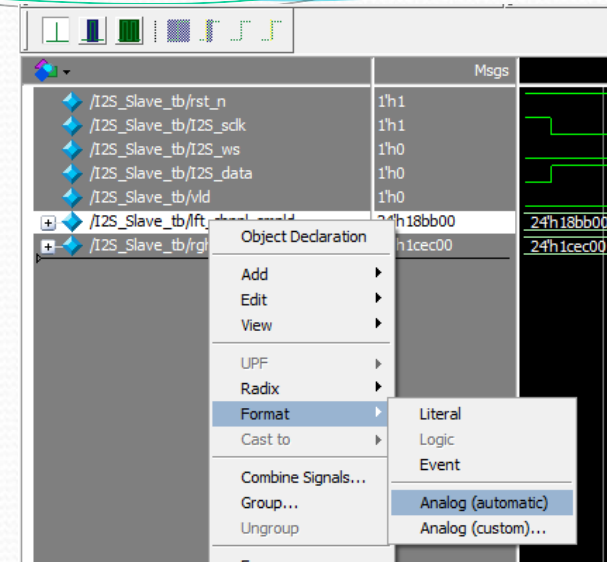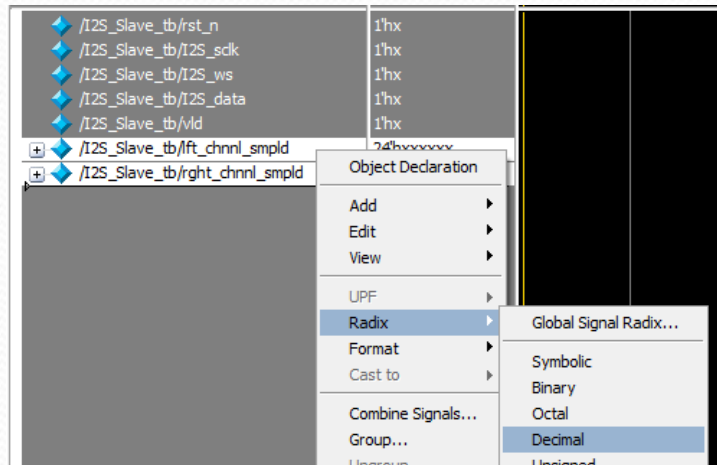

Change Radix to Decimal

 Change Format to Analog with Auto Scaling



If your I2S\_Slave is working properly then left and right channels should be sinusoidal right being a higher freq than left.

Submit whatever you have done to dropbox. Rest is due as part of HW4.